

Experiment 11

Clipper

Name: Aman Singh

Batch: EB05

Enrolment no. : E21CSEU0001

Aim:

- A. To be able to design a clipper circuit for a desired clipping value.
- B. To construct the circuit on the breadboard
- C. To observe out-put waveforms on the oscilloscope.
- D. To calculate the peak values of waveforms for positive and negative cycles.
- E. To plot input and output waveforms on a graph sheet to scale.






Apparatus required:

- Cathode Ray Oscilloscope (CRO)
- Signal generator
- Multimeter
- DC power supply
- Bread board
- Probes
- Connecting wires

Theory:


Circuit with which waveforms can be shaped by removing a portion of the signal is known as clipper circuit. There are used as limiters/slicers to chip the waveform above/ below a certain level.

Circuit Diagrams:

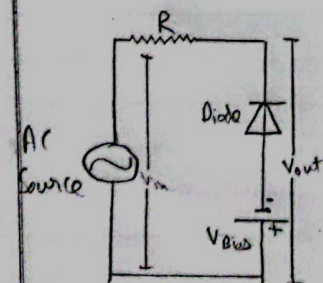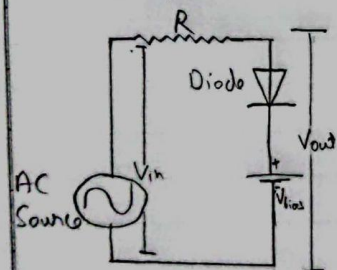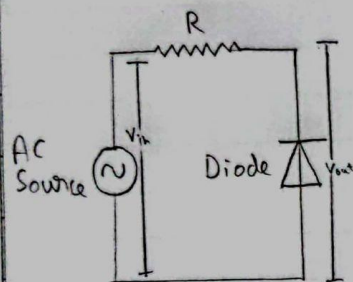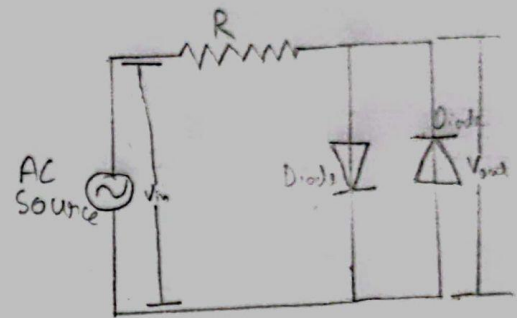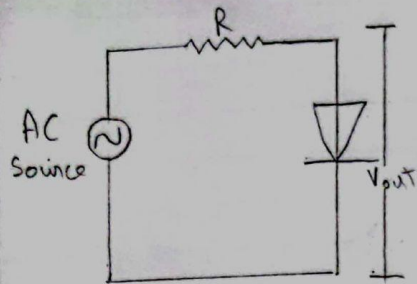


Readings with circuits in tinkercad:


For all $V_{in} = 5\text{ V}$

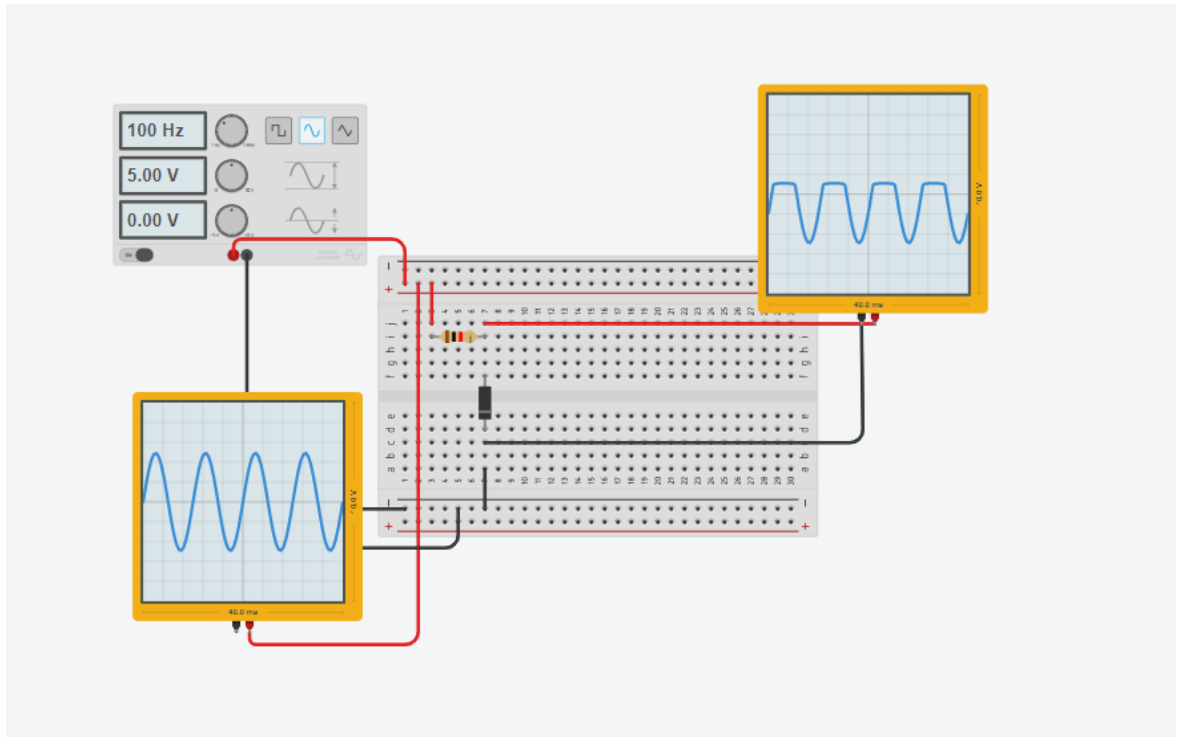


$V_{out} = 3\text{ V}$

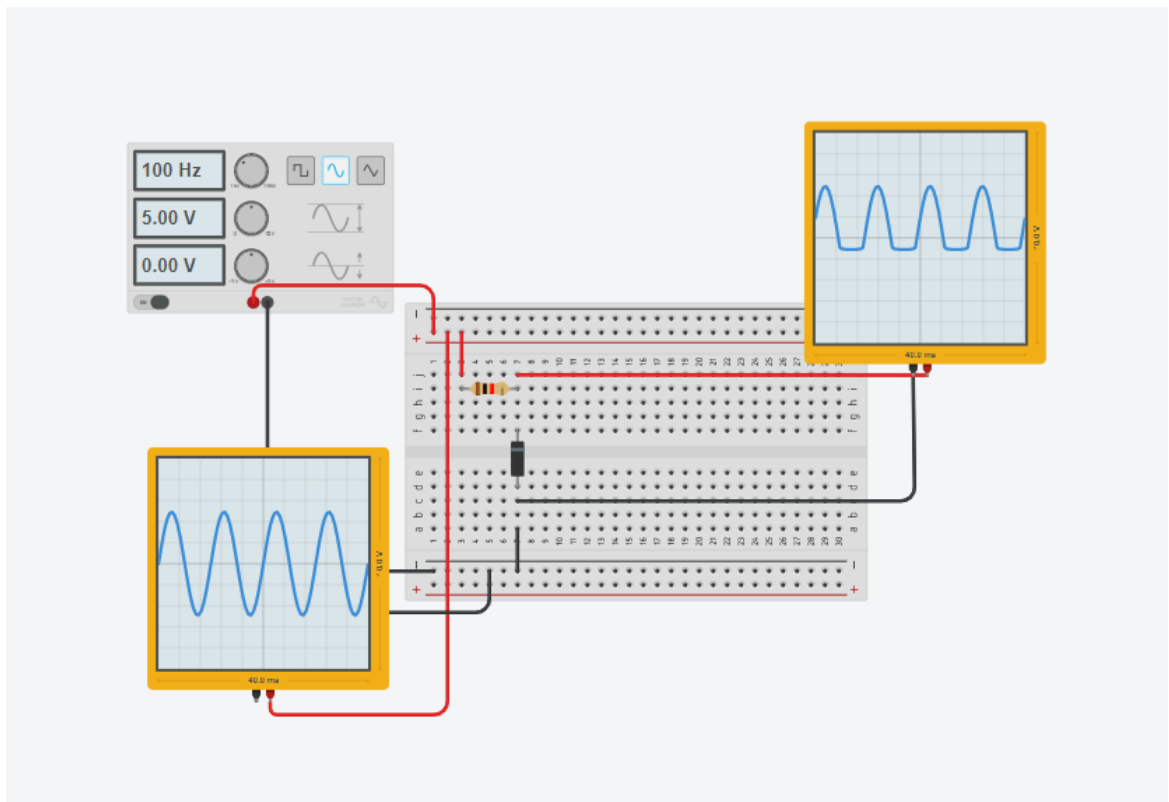


V out = 3V

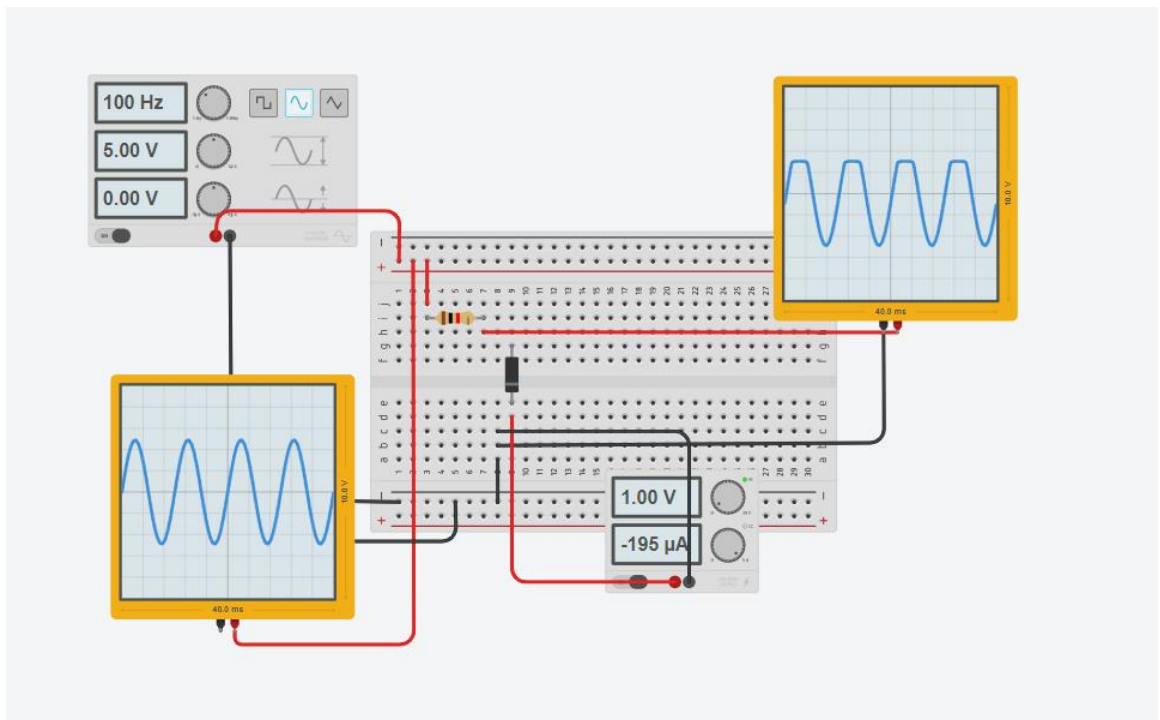

V out = 4V

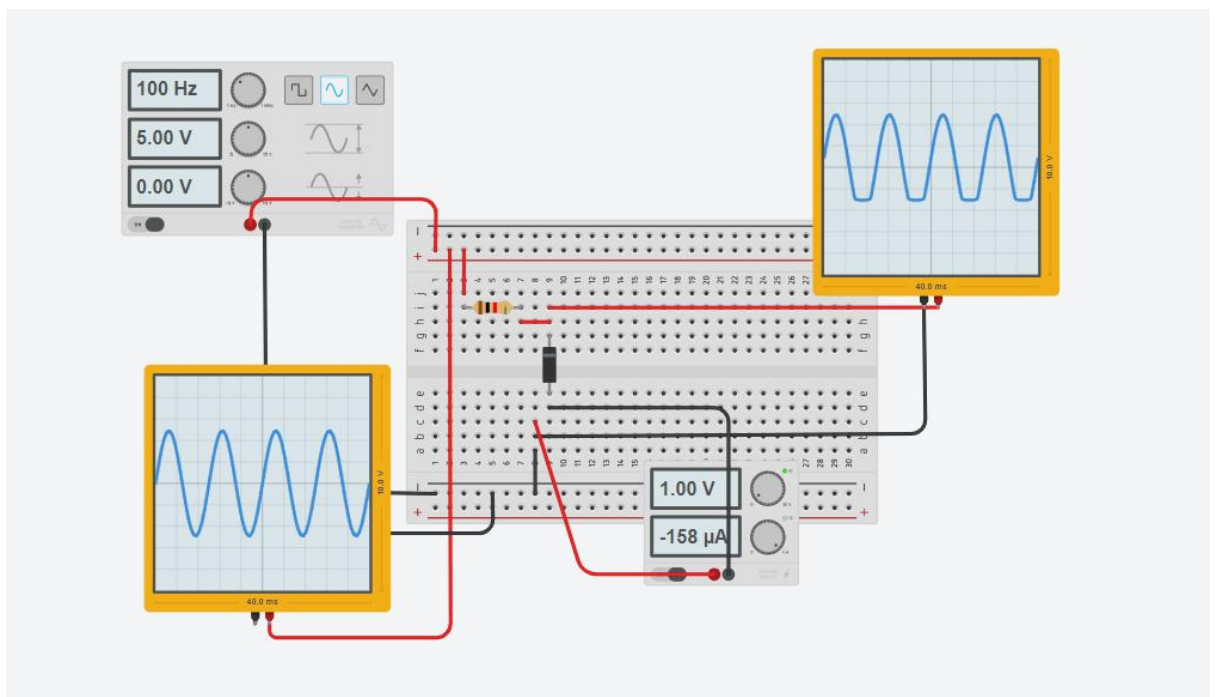



V out = 4V

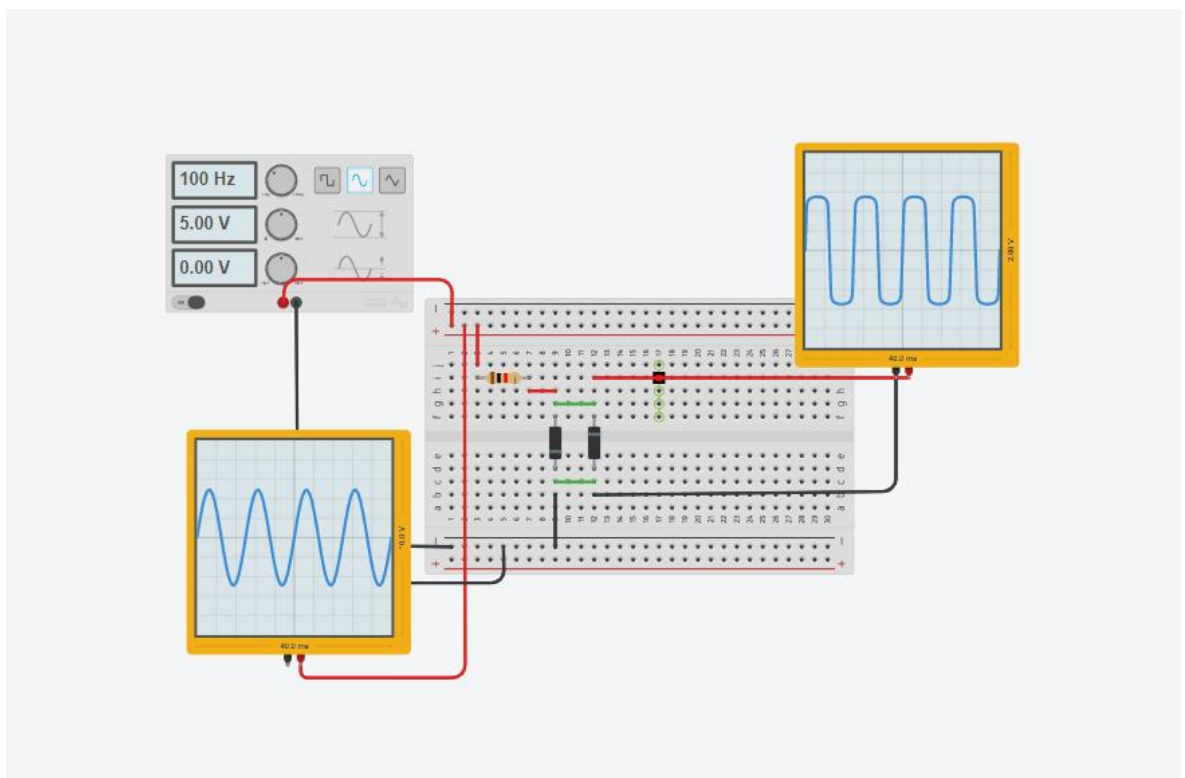

V out = 1V

Graph of Waveforms:

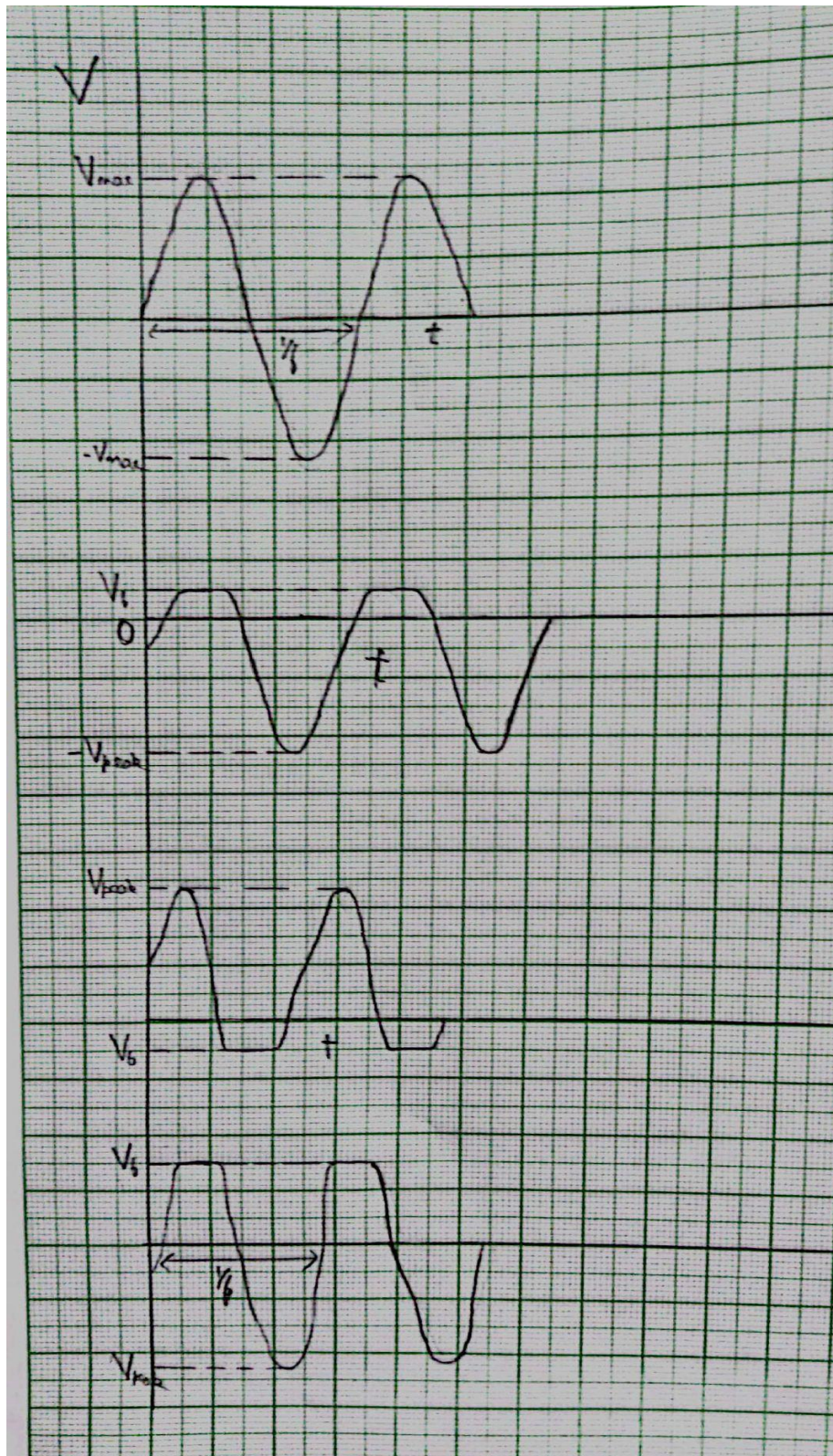

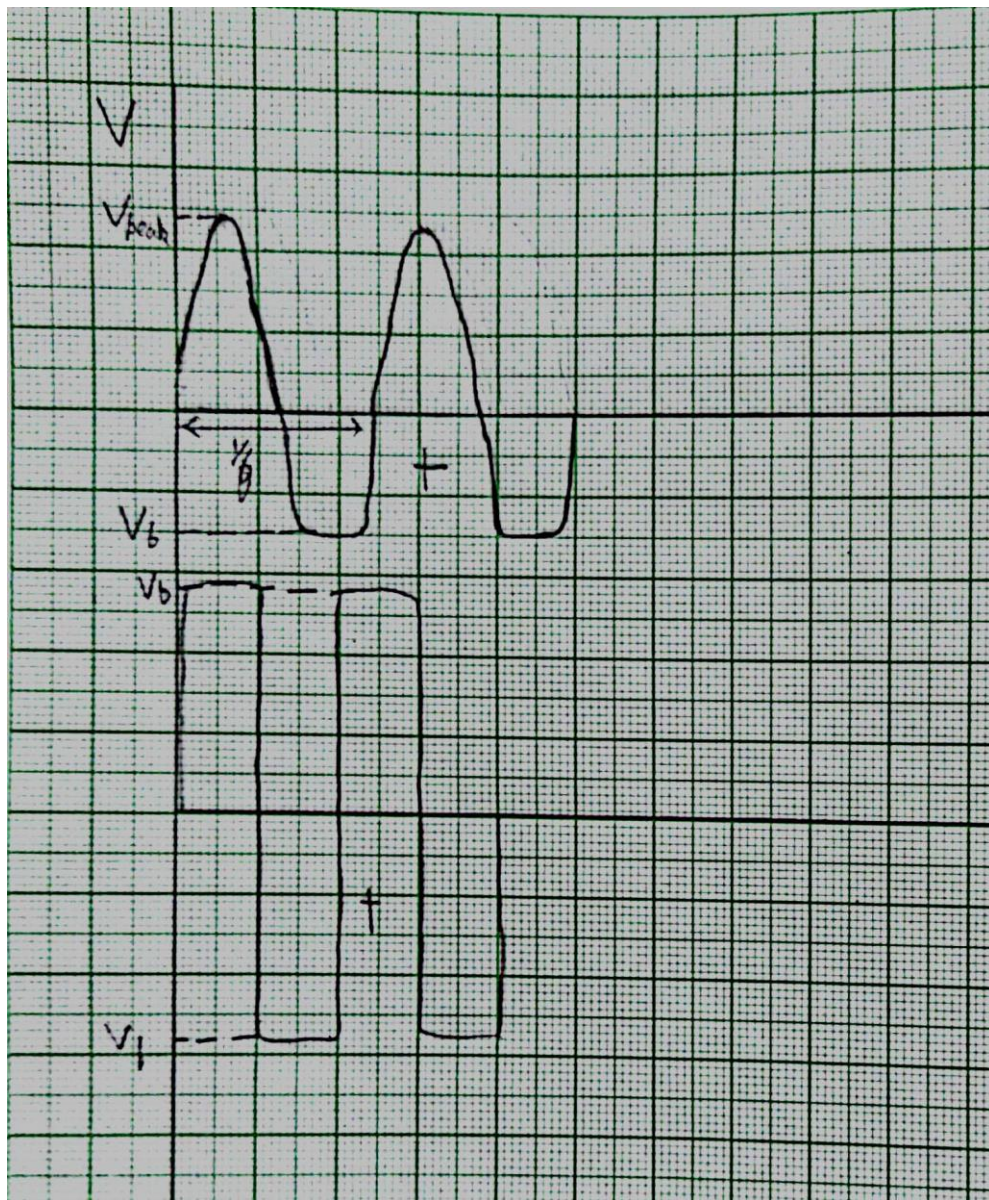

Conclusion:

The experiment made the working of different types of clipper circuits clear.